 


1-Bit Adders

Half Adder




A	B	C_{out}	S
0	0		
0	1		
1	0		
1	1		

$$S = A \oplus B$$

$$C_{out} = A \cdot B$$

Full Adder

 


C_{in}	A	B	C_{out}	S
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

$$S = A \oplus B \oplus C_{in}$$

$$C_{out} = A \cdot B + (A \oplus B) \cdot C_{in}$$

1-Bit Adders

Half Adder

 


A	B	C_{out}	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

$$S = A \oplus B$$

$$C_{out} = A \cdot B$$

Full Adder

 


C_{in}	A	B	C_{out}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$S = A \oplus B \oplus C_{in}$$

$$C_{out} = A \cdot B + (A \oplus B) \cdot C_{in}$$

1-Bit Adders

Half Adder

 


A	B	C _{out}	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

$$S = A \oplus B$$

$$C_{out} = AB$$

Full Adder

 


C _{in}	A	B	C _{out}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$S = A \oplus B \oplus C_{in}$$

$$C_{out} = AB + AC_{in} + BC_{in}$$


Multibit Adders (CPAs)

 - Types of carry propagate adders (CPAs):
 - Ripple-carry (slow)
 - Carry-lookahead (fast)
 - Prefix (faster)
- Carry-lookahead and prefix adders faster for large adders but require more hardware



Ripple-Carry Adder

 - Chain 1-bit adders together
- Carry ripples through entire chain
- Disadvantage: **slow**




Ripple-Carry Adder Delay

$$t_{\text{ripple}} = N \times t_{FA}$$


where t_{FA} is the delay of a full adder

Subtractor


Symbol

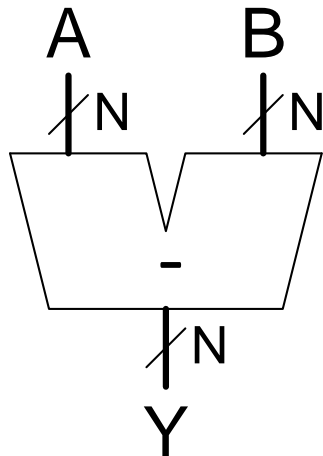

Implementation

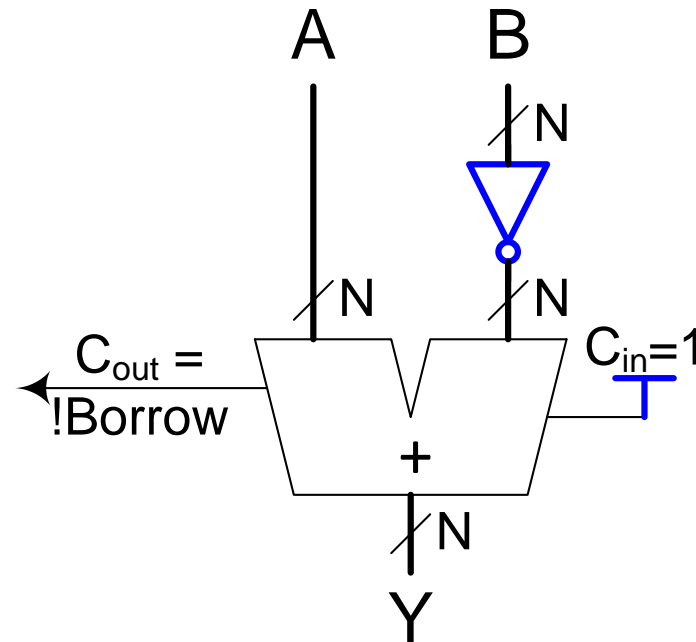

Adder/Subtractor

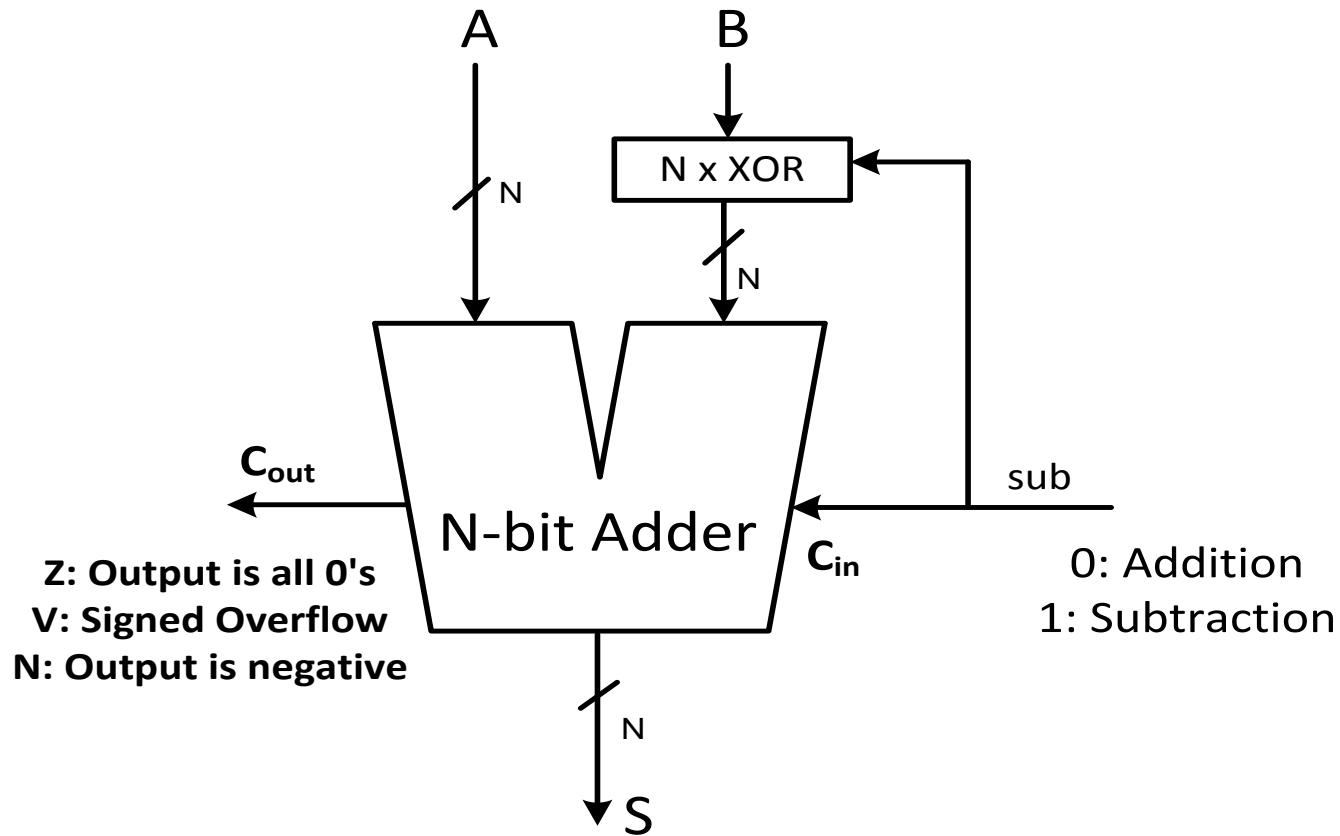

Adder/Subtractor Signed Overflow

- In signed addition, overflow occurs when:
 - positive + positive \Rightarrow negative
 - negative + negative \Rightarrow positive

positive + negative never generates an overflow
- In signed subtraction, overflow occurs when:
 - positive – negative \Rightarrow negative
 - negative – positive \Rightarrow positive

positive – positive or negative – negative
never generates an overflow

Adder/Subtractor, Unsigned Numbers

- If A and B are unsigned numbers:
 - sub = 0 means $S = A + B$
 - sub = 1 means $S = A + \sim B + 1 = A - B$
- C_{out} is addition overflow indicator:
 - If set, it shows 2^N should be added to S
- $!C_{out}$ (= Borrow) is subtraction underflow indicator:
 - If set, S is correctly equal to $S = A - B$
 - If not set, 2^N should be deducted from S
- While Z shows output is all zero, **N and V do not have any meaning** in unsigned addition/subtraction

Adder/Subtractor, Signed Numbers

- If A and B are signed numbers:
 - sub = 0 means $S = A + B$
 - sub = 1 means $S = A + \sim B + 1 = A - B$
- V is addition/subtraction overflow indicator
- Unlike unsigned addition/subtraction, output S can not be reconstructed when overflow occurs.
- Indeed, a new addition/subtraction with extra bits (recall sign-extension) are required to prevent any signed overflow
- While Z shows output is all zero, C_{out} *do not have any meaning* in signed addition and/or subtraction

Adder/Subtractor, Elaboration

- A binary adder can **blindly** add/subtract signed and unsigned numbers, thanks to the two's complement signed number representation.
 - Warning: above statement is not correct for multiplication and division.
- This is user responsibility to properly treat the output specially when an overflow occurs.
 - In unsigned numbers, C_{out} shows exact error amount.
 - In signed numbers, output should be thrown out, when V (signed overflow) is asserted.

Comparator, Unsigned Numbers

Calculate $A + \sim B + 1$ (i.e. Subtract)

$A == B$

$A == B$	

Comparator, Unsigned Numbers

Calculate $A + \sim B + 1$ (i.e. Subtract)

$A == B$

Z

$A != B$

!Z

Comparator, Unsigned Numbers

Calculate $A + \sim B + 1$ (i.e. Subtract)

$A == B$

Z

$A != B$

!Z

$A >= B$

Comparator, Unsigned Numbers

Calculate $A + \sim B + 1$ (i.e. Subtract)

$A == B$

Z

$A != B$

!Z

$A >= B$

C_{out}

$A < B$

! C_{out}

Comparator, Unsigned Numbers

Calculate $A + \sim B + 1$ (i.e. Subtract)

$A == B$

Z

$A != B$

!Z

$A \geq B$

C_{out}

$A < B$

! C_{out}

$A > B$

Comparator, Unsigned Numbers

Calculate $A + \sim B + 1$ (i.e. Subtract)

$A == B$

Z

$A != B$

$!Z$

$A >= B$

C_{out}

$A < B$

$!C_{out}$

$A > B$

$C_{out} \& !Z$

$A <= B$

$!C_{out} | Z$

Comparator, Signed Numbers

Calculate $A + \sim B + 1$ (i.e. Subtract)

$A == B$

$A == B$	

Comparator, Signed Numbers

Calculate $A + \sim B + 1$ (i.e. Subtract)

$A == B$

Z

$A != B$

!Z

Comparator, Signed Numbers

Calculate $A + \sim B + 1$ (i.e. Subtract)

$A == B$

Z

$A != B$

!Z

$A >= B$

Comparator, Signed Numbers

Calculate $A + \sim B + 1$ (i.e. Subtract)

$A == B$

Z

$A != B$

$!Z$

$A >= B$

$(!N \& !V) | (N \& V)$

$A < B$

$N \text{ xor } V$

Comparator, Signed Numbers

Calculate $A + \sim B + 1$ (i.e. Subtract)

$A == B$

Z

$A != B$

!Z

$A >= B$

$(!N \& !V) | (N \& V)$

$A < B$

$N \text{ xor } V$

$A > B$

Comparator, Signed Numbers

Calculate $A + \sim B + 1$ (i.e. Subtract)

$A == B$

Z

$A != B$

$!Z$

$A >= B$

$(!N \& !V) | (N \& V)$

$A < B$

$N \text{ xor } V$

$A > B$

$(N \text{ xnor } V) \& !Z$

$A <= B$

$(N \text{ xor } V) | Z$

Comparator, Elaboration

- For unsigned numbers, an n-bit binary adder/subtractor in subtraction mode can compare two n-bit unsigned numbers:

ONLY look at C_{out} (= ! Borrow) and Z

- For signed numbers, above binary subtractor can compare two n-bit signed numbers, even when a signed overflow occurs and output S should be discarded:

When $V = 0$, look at N

When $V = 1$, N is complemented, thus look at ! N